

METE 3100U  
Actuators and Power Electronics

Lecture 3  
Transformers


# Outline of Lecture 3

In today's lecture we will

- Review the principles of transformers
- Model and analyse a transformer
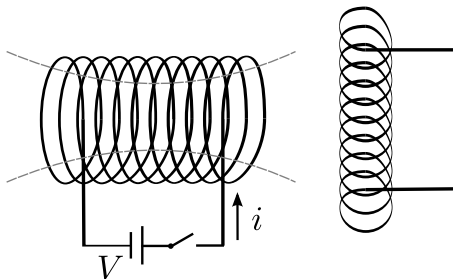
## Faraday's law - from lecture 1


A change in the magnetic environment of a coil will cause a voltage (emf) to be induced in the coil



Electromotive force (EMF): drives a current in electrical circuits
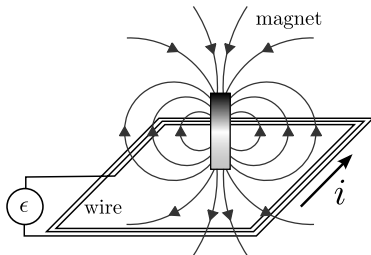
## Lenz's law - from lecture 2

An induced electromotive force  $\epsilon$  gives rise to a current  $i$  whose magnetic field opposes the change in original magnetic flux.




Lenz's law is shown with the negative sign in Faraday's law of induction

$$\epsilon = -N \frac{\partial \Phi}{\partial t} \quad (1)$$

Ohm's law yields:

$$\epsilon = iR \quad (2)$$

# Ideal transformer

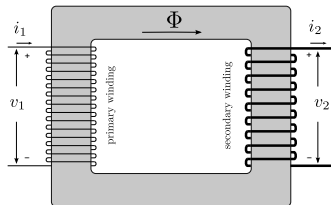


$$v_1 = \epsilon_1 = N_1 \frac{d\Phi}{dt}, \quad v_2 = \epsilon_2 = N_2 \frac{d\Phi}{dt} \quad (3)$$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} = a \quad (4)$$

- Windings have zero resistance and inductance
- No flux leakage
- The permeability of the core is infinite (zero reluctance)

## Ideal transformer

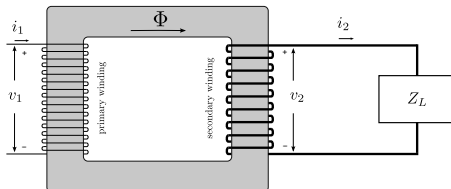

When a load  $Z_L$  is attached, a current  $i_2$  flow in the secondary coil.

$$\sum \epsilon = 0 \rightarrow N_1 i_1 - N_2 i_2 = 0 \quad (5)$$


$$\frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a} \quad (6)$$

The instantaneous power is conserved:

$$v_1 i_1 = v_2 i_2 \quad (7)$$

$v$  is the root mean square of a sinusoidal voltage.

## Impedance transfer

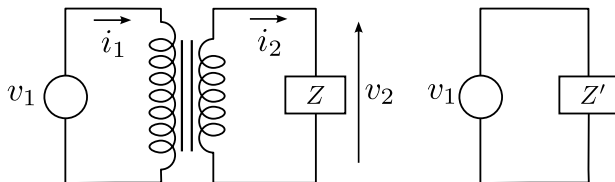


$$Z_2 = \frac{V_2}{i_2}, \quad Z_1 = \frac{V_1}{i_1} \quad (8)$$

Since  $V_1 = V_2 a$ , and  $i_1 = i_2 / a$ , the input impedance becomes

$$Z_1 = \frac{V_2 a}{i_2 / a} = a^2 \frac{V_2}{i_2}$$
$$Z' =$$

## Practical transformer

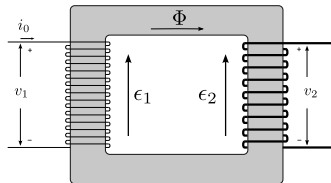


The no-load current  $i_0$ :

→ Magnetizes the transformer's core ( $i_\phi$ )

→ Compensates the magnetic losses such as eddy current ( $i_R$ )

$$\Phi(t) = \Phi_{\max} \sin(\omega t)$$
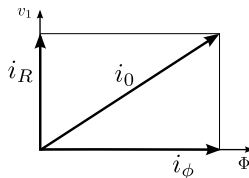
$$v_1(t) = N \frac{d\Phi}{dt} = N \Phi_{\max} \omega \cos(\omega t)$$





## Practical transformer


The inductance  $L$  of the windings is defined as the flux linkage  $\lambda$  of the coil per Ampère of its current.

Flux linkage:  $N$  times the magnetic flux:

$$\lambda = N\Phi \quad (9)$$

From Lenz' law, the inductance is a property of a conductor which opposes any change in current through the conductor:

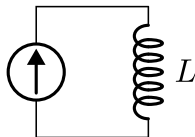
$$L = \frac{\lambda}{i} = \frac{N\Phi}{i} \quad (10)$$




$$L = \frac{NBA}{i} = \frac{N\mu HA}{i} = \frac{NBA}{\frac{H\ell}{N}} = \frac{N^2}{\frac{\ell}{\mu A}} \quad (11)$$

$$L = \frac{N^2}{\Re} \quad (12)$$


## Equivalent circuit

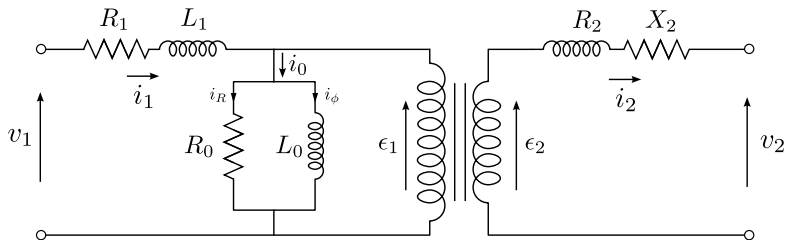

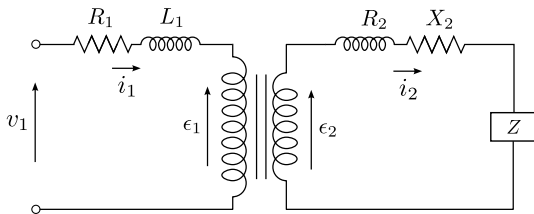
If the transformer is loaded, then  $i_1 \gg i_0$ :



## Equivalent circuit

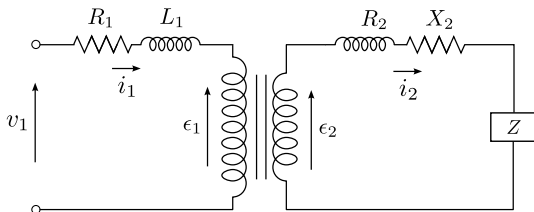

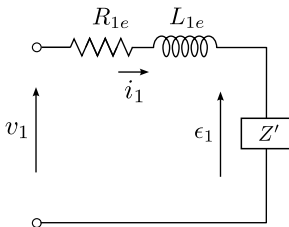Secondary impedance referred to the primary




$$R_{1e} = R_1 + R_2 \left( \frac{N_1}{N_2} \right)^2$$


$$L_{1e} = L_1 + L_2 \left( \frac{N_1}{N_2} \right)^2$$

$$Z' = Z \left( \frac{N_1}{N_2} \right)^2$$

## Equivalent circuit

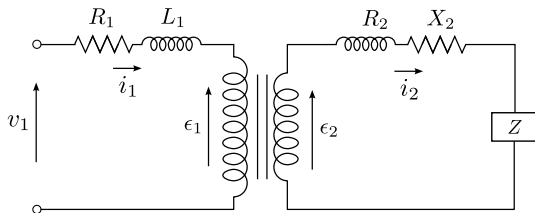

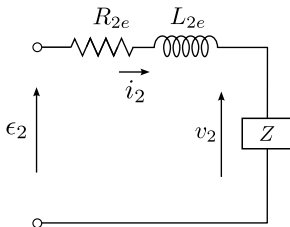Primary impedance referred to the secondary



$$R_{2e} = R_2 + R_1 \left( \frac{N_2}{N_1} \right)^2$$

$$L_{2e} = L_2 + L_1 \left( \frac{N_2}{N_1} \right)^2$$

## Transformer rating

→ Kilovolt-Ampère (kVa): 10 kVA, 1100/110

→ Primary:  $v_1 = 1100 \text{ V}$ ,

→ Secondary:  $v_2 = 110 \text{ V}$ ,

→ Turn ratio:  $a = 1100/110 = 10$

Input current:

Output current:

Note that in practice  $i_0 \neq 0$



## Exercise 04

Circuit tests performed on a 10 kVA, 2200/220 V, 60 Hz transformer as follows:

→ Test 1 - No load test: The terminals of the high voltage side are open

→ Test 2 - Short circuit test: The terminals of the low voltage side are shorted


The obtained results are:

	Test 1	Test 2
Applied voltage	220 V	150 V
Input current	2.5 A	4.55 A
Dissipated power	100 W	215 W


Determine the parameters for the approximate equivalent circuits referred to the low-voltage side and the high-voltage side.

## Exercise 04 - continued

### Step 1: No-load test

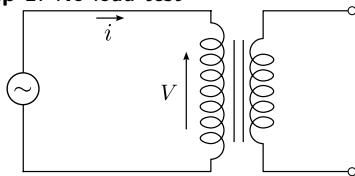


no-load circuit test

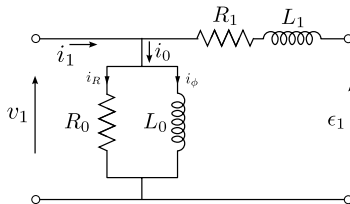


no-load equivalent circuit

## Exercise 04 - continued

### Step 2: Short circuit test

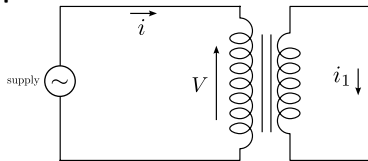

short circuit test

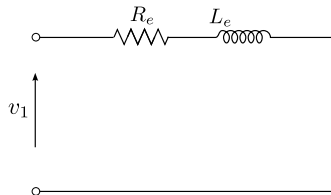


equivalent shorted circuit



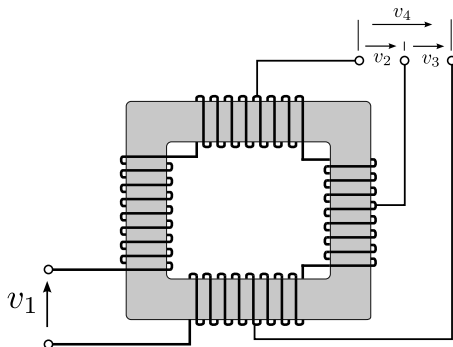
# Autotransformers

- Allows for a variable AC voltage at the secondary.
- The primary and secondary are connected.




Note that  $v_2 \approx v_3 < v_4 < v_1$

# Autotransformers

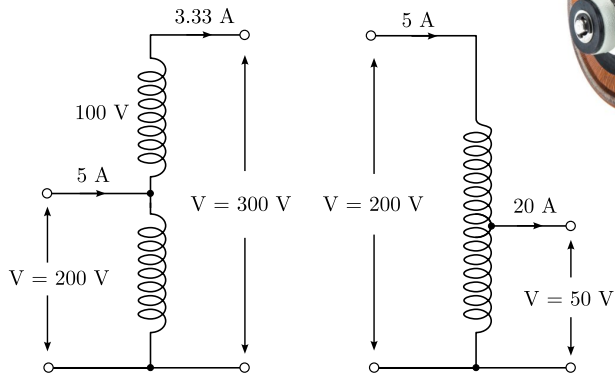


# Experiment - Jacob's ladder

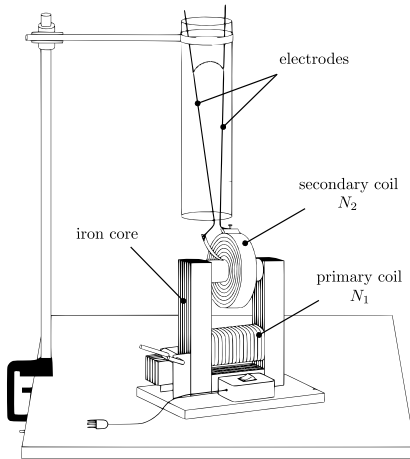

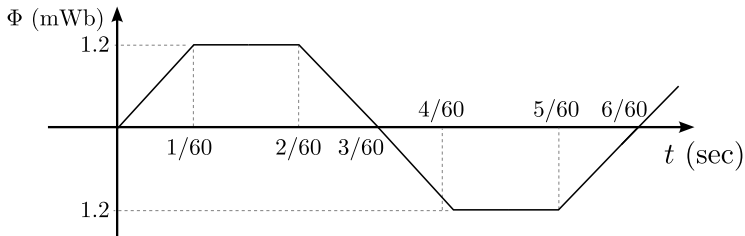
## Exercise 05

The flux in a single phase transformer varies with time as shown in the graph. The primary coil has 400 turns and the secondary coil has 100 turns. Sketch the waveform of the induced voltage  $e_1$  in the primary winding.




## Exercise 05 - continued

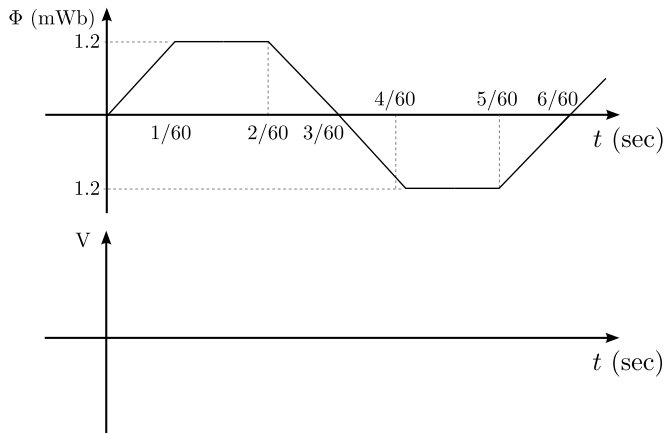


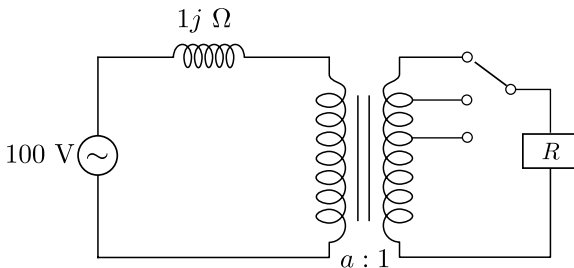
## Exercise 06

A resistive load varies from 1 to  $0.5\ \Omega$ . The generator can be modelled as an ideal transformer with a constant voltage of 100 V in series with an inductive reactance. For maximum power transfer to the load, the effective load resistance seen at the transformer primary must equal the series impedance of the generator, that is, the referred value of  $R$  to the primary side is always  $1\ \Omega$ .




Determine the turn ratio and the load voltage for maximum power transfer.

## Exercise 06 - continued

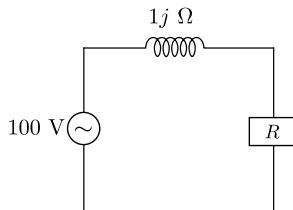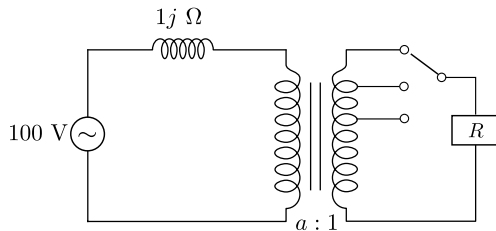


## Exercise 06 - continued

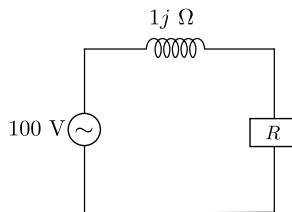




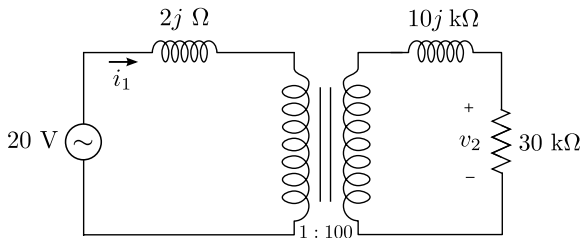
## Exercise 07


For the circuit shown, consider the transformer to be ideal with a turn ratio of 1:100. Calculate the actual load voltage  $v_2$  and the supply current  $i_1$ .



## Exercise 07 - continued

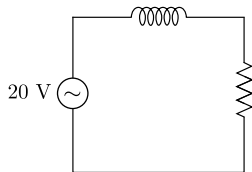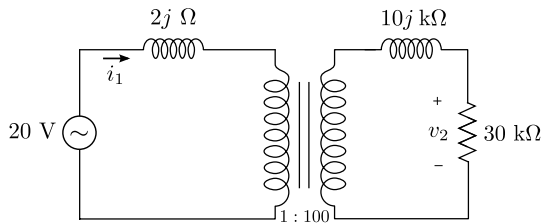


## Exercise 07 - continued

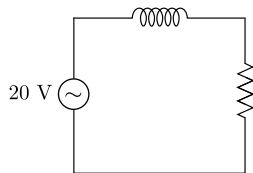

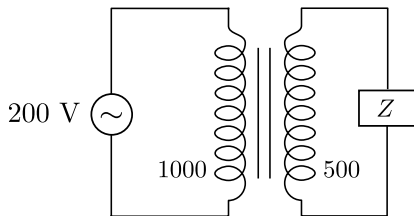
## Exercise 08

The transformer has 1000 turns on the primary and 500 turns on the secondary. The primary winding is connected to a 200 V supply and the secondary winding is connected to a 5 kVA load. The transformer can be considered as ideal.



- (a) Determine the load voltage
- (b) Determine the load impedance
- (c) Determine the load impedance referred to the primary

## Exercise 08 - continued

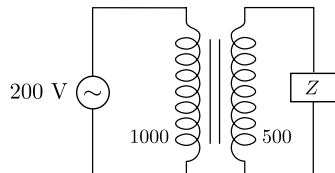

## Exercise 09

A single phase transformer has 500 turns in the primary winding. When it is connected to a 120 V, 60 Hz power supply, the no-load current is 1.6 A and the no-load power is 80 W. Neglect the winding resistance and leakage reactance of the winding. Calculate

- (a) The core loss current  $i_c$
- (b) The magnetizing current  $i_m$
- (c) The peak value of the core flux  $\Phi_m$

## Exercise 09 - continued

## Next class...

- Diode rectifiers (AC/DC converter)

Additional supporting materials for Lecture 3:

Transformer loading: <https://goo.gl/kRnViR>

Autotransformer inner workings: <https://goo.gl/zCQf9j>

Three-phase transformer: <https://goo.gl/8Ddw2C>