

METE 3100U
Actuators and Power Electronics

Lecture 6
DC/AC Converters


Outline of Lecture 6

In today's lecture we will

- Understand the principles of DC/AC converters
- Analyse and design DC/AC converters
- Understand the principles of voltage modulation


Applications

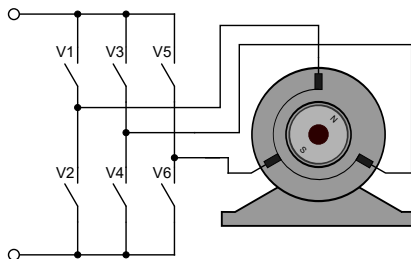Inverter circuits designed to produce a variable output voltage range are often used within motor speed controllers.




Applications

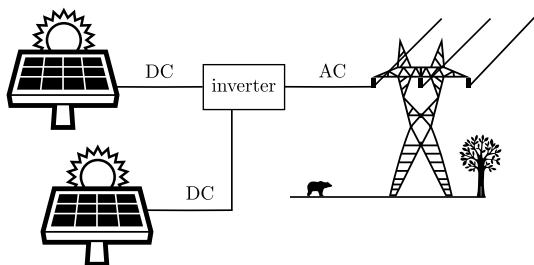A solar inverter converts the DC output of a solar panel into a utility frequency AC current that can be fed into a commercial electrical grid.



Half bridge inverter

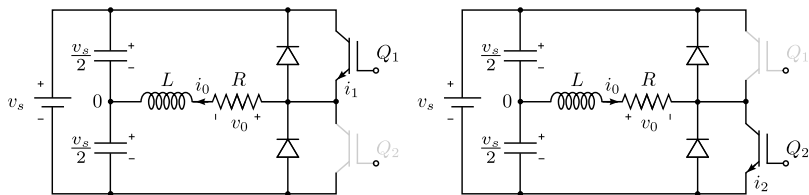

Q_1 on, Q_2 off: the voltage across the load is

$$v_0 = \quad (1)$$


Q_2 on, Q_1 off: the voltage across the load is

$$v_0 = \quad (2)$$

Q_1 and Q_2 on: the voltage across the load is

$$v_0 = \quad (3)$$


DC/AC converters

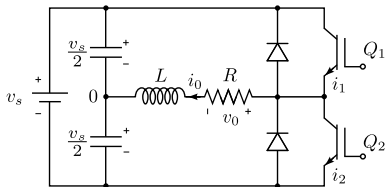

The root mean square of the output voltage is


$$v_0 = \sqrt{\frac{1}{T} \int_0^T v_0^2 dt}$$
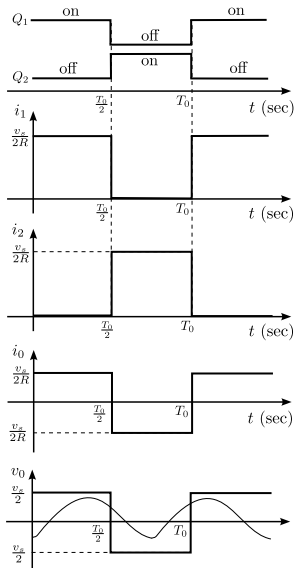
$$v_0 = \sqrt{\frac{1}{T} \int_0^T \left(\frac{v_s}{2}\right)^2 dt} = \frac{v_s}{2}$$



Fundamental harmonics

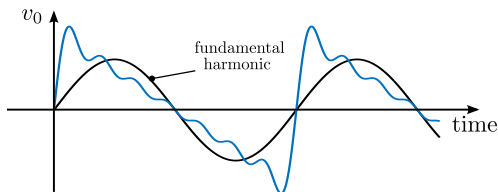A harmonic is a voltage or current at a multiple of the fundamental frequency, produced by the action of non-linear loads such as voltage converters.



Using a Fourier series, the load voltage is

$$v_0 = \frac{a_0}{2} + \sum_{n=1}^{\infty} [a_n \cos(n\omega t) + b_n \sin(n\omega t)] \quad (4)$$

Due to symmetry around the x-axis, $a_0 = a_n = 0$.

Fundamental harmonics

We get b_n as

$$b_n = \frac{1}{n} \left[\int_{-\frac{\pi}{2}}^0 -\frac{v_s}{2} \sin(n\omega t) d(\omega t) + \int_0^{\frac{\pi}{2}} \frac{v_s}{2} \sin(n\omega t) d(\omega t) \right] = \frac{2v_s}{n\pi} \quad (5)$$

Thus the instantaneous output voltage is

$$v_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2v_s}{n\pi} \sin(n\omega t) \quad (6)$$

For $n = 1$, the rms voltage of the fundamental component is

$$V_{r1} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{2v_s}{\pi} \sin(\omega t) \right)^2 dt} \quad (7)$$

where the frequency ω in **rad/s** is

$$\omega = \frac{2\pi}{T} \quad (8)$$



Fundamental harmonics

$$V_{r1}^2 = \frac{1}{T} \frac{4v_s^2}{\pi^2} \int_0^T \left(\frac{1}{2} - \frac{\cos(2\omega t)}{2} \right) dt \quad (9)$$

After some straightforward manipulation

$$V_{r1} = \frac{2v_s}{\pi\sqrt{2}} = 0.45v_s \quad (10)$$

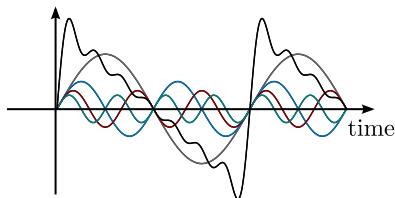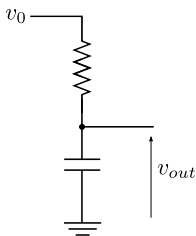v_0 may require filtering to eliminate higher harmonics



Half-bridge with RL load

For an LR load, the impedance is

$$Z = R + jn\omega L \quad (11)$$

The load current is

$$i_0 = \frac{v_0}{Z} \quad (12)$$

which gives

$$i_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2v_s}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n) \quad (13)$$

with $\theta_n = \tan^{-1} \left(\frac{n\omega L}{R} \right)$

The fundamental output power ($n = 1$) is

$$P = (V_{r1})(I_{r1}) \cos(\theta_n) = I_{r1}^2 R \quad (14)$$

Half-bridge with RL load

I_{r1} is the rms current of the first harmonic:

$$I_{r1} = \frac{2v_s}{\pi\sqrt{2}\sqrt{R^2 + (\omega L)^2}} \quad (15)$$

Thus the output power is

$$P_{r1} = \left[\frac{2v_s}{\pi\sqrt{2}\sqrt{R^2 + (\omega L)^2}} \right]^2 R \quad (16)$$

Higher harmonic ($n > 1$) are dissipated as heat.

Assuming a lossless inverter

$$\int_0^T v_s(t)i_s(t)dt = \int_0^T v_0(t)i_0(t)dt \quad (17)$$

Supply current

For high L and ω , i_0 is nearly sinusoidal and only the fundamental component provides power to the load:

$$\int_0^T v_s(t) i_s(t) dt = \int_0^T V_{r1} I_{r1} \cos(\theta_1) dt \quad (18)$$

v_s remains constant, thus the supply current is

$$I_s T = \frac{1}{v_s} \int_0^T V_{r1} I_{r1} \cos(\theta_1) dt \quad (19)$$


$$I_s = \frac{V_{r1}}{v_s} I_{r1} \cos(\theta_1) \quad (20)$$

→ V_{01} is the fundamental rms output voltage

→ I_{01} is the fundamental rms load current

→ θ_1 is the load angle for $n = 1$

Gating sequence

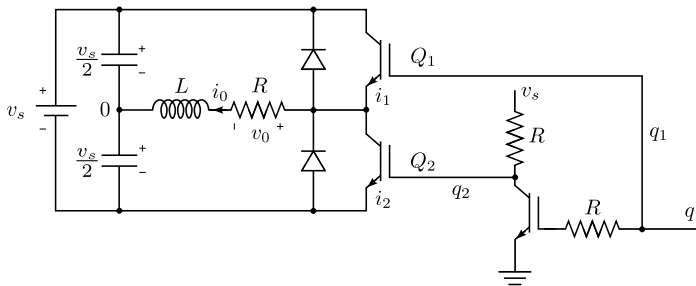


→ Generate a square-wave gating signal q_1

→ q_2 should be the logic inverter of q_1


What is the function of the diodes?

Full bridge inverters

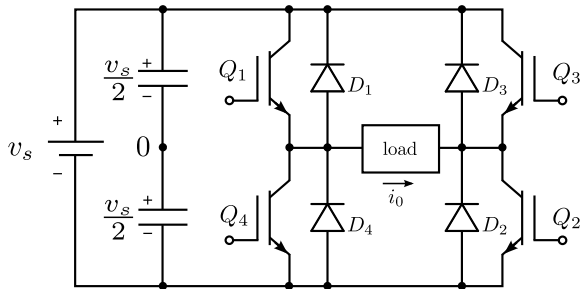

Full bridge inverters

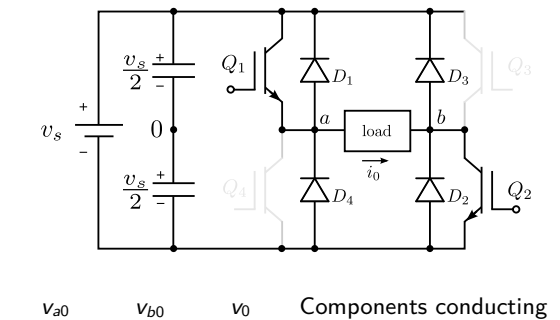State 1 - Q_1 and Q_2 are on, Q_3 and Q_4 are off




Q_1, Q_2 if $i_0 > 0$

D_1, D_2 if $i_0 < 0$

Full bridge inverters

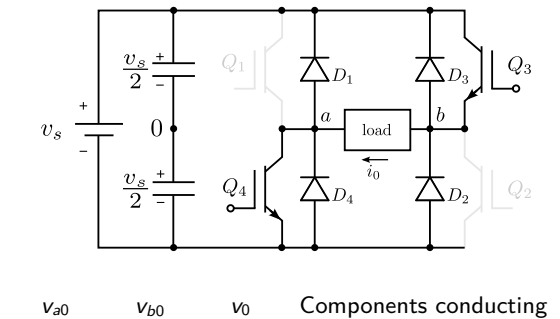State 2 - Q_3 and Q_4 are on, Q_1 and Q_2 are off




D_4, D_3 if $i_0 > 0$

Q_1, Q_3 if $i_0 < 0$

Full bridge inverters

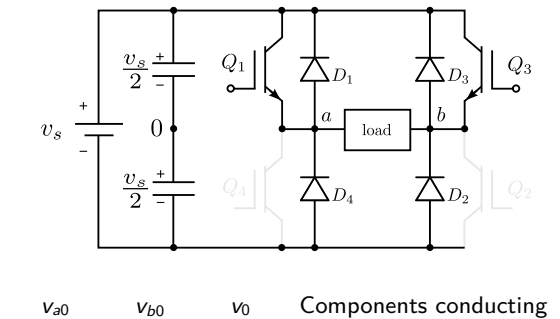
State 3 - Q_1 and Q_3 are on, Q_2 and Q_4 are off



$$S_1, D_3 \text{ if } i_0 > 0$$
$$D_1, Q_3 \text{ if } i_0 < 0$$

Full bridge inverters

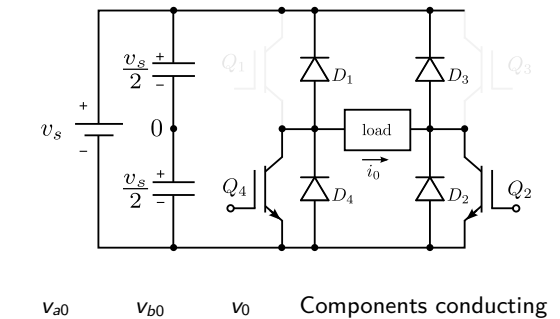State 4 - Q_2 and Q_4 are on, Q_1 and Q_3 are off




D_4, Q_2 if $i_0 > 0$

Q_4, D_2 if $i_0 < 0$

Full bridge inverters


State 5 - All switches are off

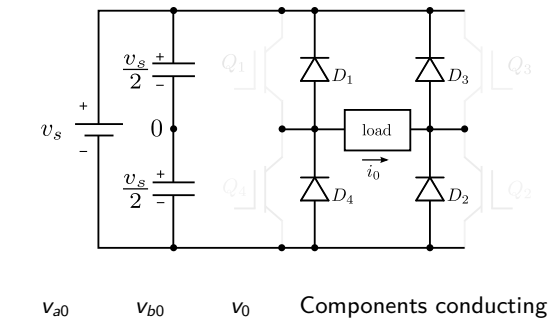

$$D_4, D_3 \text{ if } i_0 > 0$$

$$D_1, D_2 \text{ if } i_0 < 0$$

Gating sequence

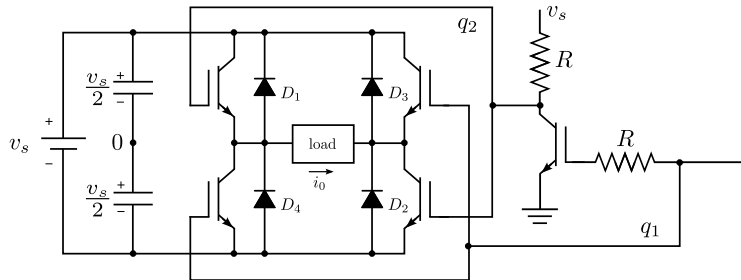

- Generate a square-wave gating signal q_1
- q_2 should be the logic inverter of q_1

Full bridge inverter

The rms output voltage is

$$v_0 = \sqrt{\frac{1}{T} \int_0^T v_s^2 dt} = v_s \quad (21)$$

Following the same procedure as for the half-bridge:

$$v_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4v_s}{n\pi} \sin(n\omega t) \quad (22)$$

The fundamental component is

$$V_{1r} = \frac{4v_s}{\pi\sqrt{2}} = 0.9v_s \quad (23)$$

For an RL load, the **instantaneous** current is

$$i_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4v_s}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n) \quad (24)$$

with $\theta_n = \tan^{-1} \left(\frac{n\omega L}{R} \right)$

Measures of performance

Harmonic factor: The individual harmonic contribution

$$HF_n = \frac{V_{rn}}{V_{r1}} \quad (25)$$

V_{rn} is the n^{th} rms harmonic component

Harmonic distortion: Closeness between a waveform and its fundamental component


$$THD = \frac{1}{V_{1r}} \sqrt{\sum_{n=3,5,7,\dots}^{\infty} V_{on}^2} \quad (26)$$

Distortion factor: Harmonics remaining after filtering

$$DF = \frac{1}{V_{1r}} \sqrt{\sum_{n=3,5,7,\dots}^{\infty} \left(\frac{V_{on}}{n^2}\right)^2} \quad (27)$$

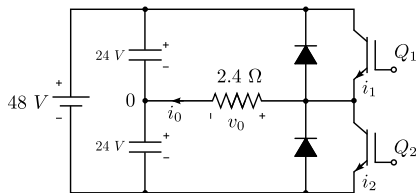Exercise 20


Consider the following single phase half bridge inverter with a resistive load of $R = 2.4 \Omega$



Determine:

- The rms output voltage at the fundamental frequency
- The output power
- The average and peak current of each transistor for a 50% duty cycle
- The average supply current I_s


Exercise 20 - continued

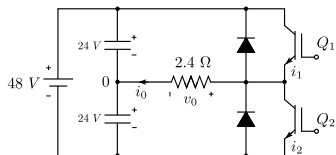

(a) The rms output voltage at the fundamental frequency

(b) The output power

Exercise 20 - continued

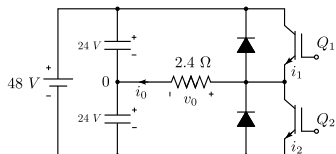


(c) The average and peak current of each transistor for a 50% duty cycle

(d) The average supply current I_s

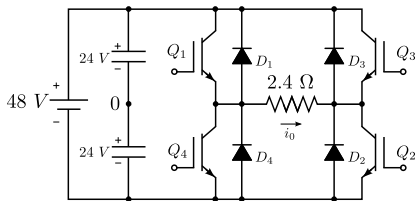Exercise 21


Consider the following single phase full bridge inverter with a resistive load of $R = 2.4 \Omega$



Determine:

- The rms output voltage at the fundamental frequency
- The output power
- The average and peak current of each transistor for a 50% duty cycle
- The average supply current I_s
- The harmonic distortion and harmonic factor


Exercise 21 - continued

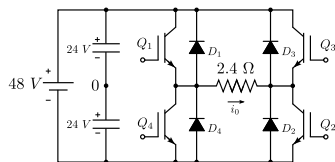

(a) The rms output voltage at the fundamental frequency

(b) The output power


Exercise 21 - continued

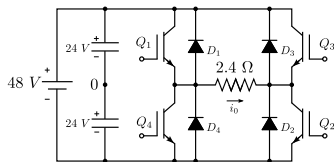

(c) The average and peak current of each transistor for a 50% duty cycle

(d) The average supply current I_s

Exercise 21 - continued

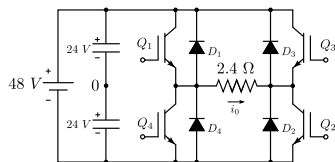


(e) The harmonic distortion and harmonic factor

Exercise 21 - continued

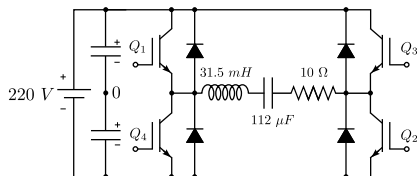
Exercise 22

Consider the following single phase full bridge inverter with a LRC load. The switching frequency is 60 Hz.



- Express the instantaneous load current as a Fourier series
- Calculate the rms load current at the fundamental frequency
- Calculate the peak and rms load current
- The load power and the fundamental output power
- The average supply current


Exercise 22 - continued

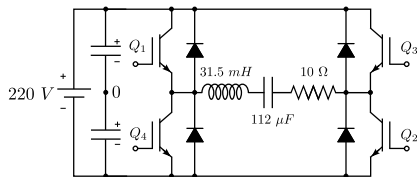

(a) Express the instantaneous load current as a Fourier series

Exercise 22 - continued


Exercise 22 - continued

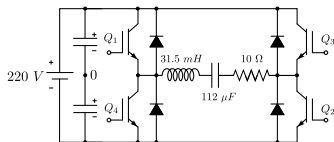

(b) Calculate the rms load current at the fundamental frequency

(c) Calculate the peak and rms load current

Exercise 22 - continued

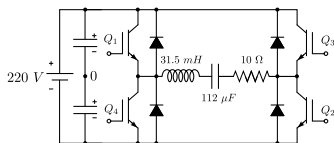


(d) The load power and the fundamental output power

(e) The average supply current

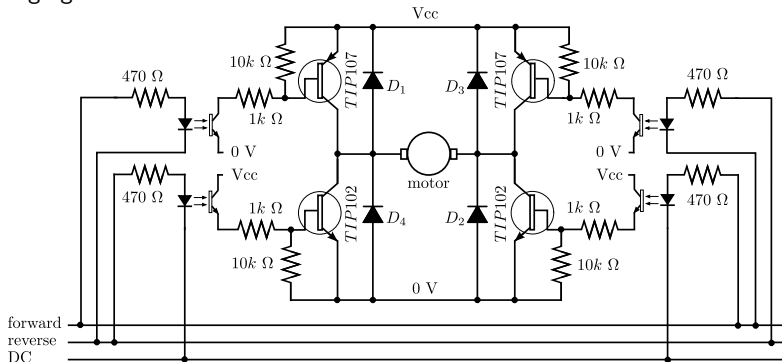Exercise 23

The full bridge inverter is used to control a DC motor using the configuration shown. Each PNP transistor is activated using an opto-isolator - an electronic component that transfers electrical signals between two isolated circuits by using light.




Describe the working of the inverter as a function of the "forward", "reverse", and duty-cycle "DC" signals.

Exercise 23 - continued


Datasheets

Opto-couplers: <https://goo.gl/BQV5B9>


Transistors: <https://goo.gl/6SBMmZ>

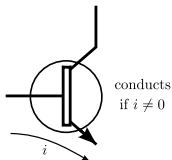

TIP102

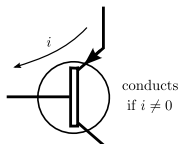


TIP107

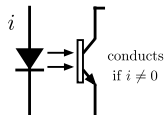

PS2501


Exercise 23 - continued

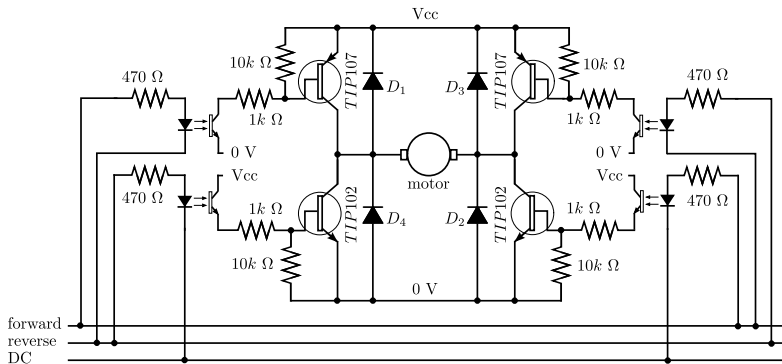

Description

Forward	1
Reverse	0
DC	


Exercise 23 - continued

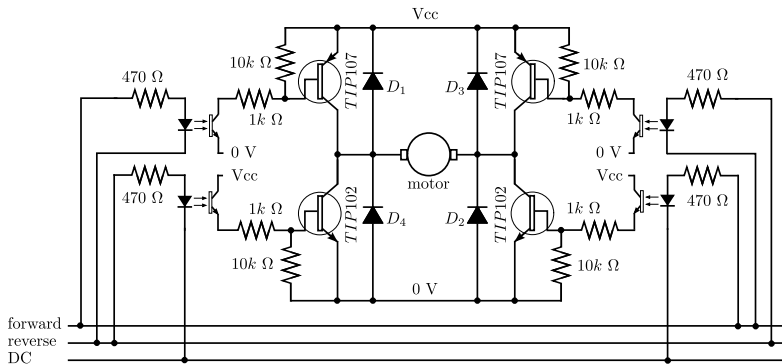

Description

Forward	0
Reverse	1
DC	


Exercise 23 - continued

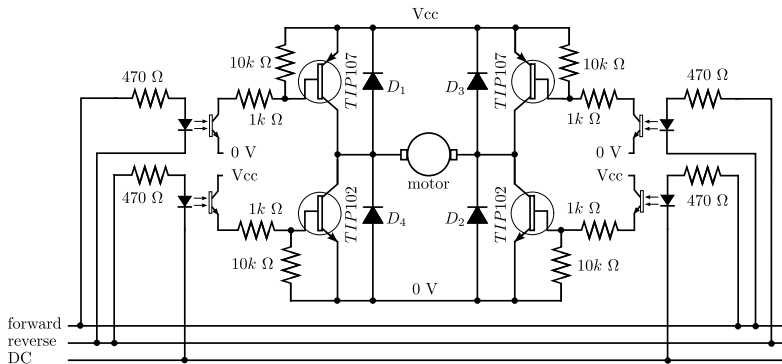

Description

Forward 0
 Reverse 0
 DC

Exercise 23 - continued

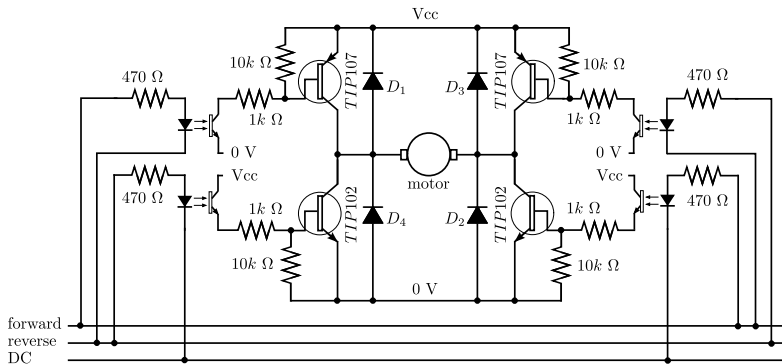


Description

Forward 1
 Reverse 1
 DC

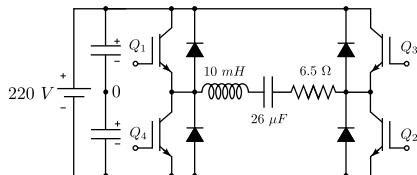Exercise 24

Consider the following single phase full bridge inverter with a LRC load. The switching frequency is 400 Hz.




- Express the instantaneous load current as a Fourier series
- Calculate the rms load current at the fundamental frequency
- Calculate the peak and rms load current
- The load power and the fundamental output power
- The average supply current

Exercise 24 - continued

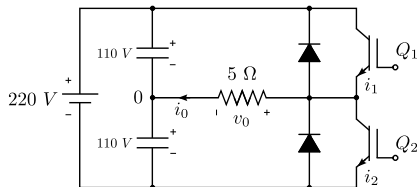Exercise 25

Consider the following single phase half bridge inverter with a resistive load of $R = 5 \Omega$



Determine:

- The rms output voltage at the fundamental frequency
- The output power
- The average and peak current of each transistor for a 50% duty cycle
- The average supply current I_s
- The harmonic distortion and harmonic factor

Exercise 25 - continued

Next class...

- Pulse width modulation

Additional supporting materials for Lecture 6:

DC/AC converters: <https://goo.gl/poscjj>

H-bridge motor control: <https://goo.gl/VVFmDc>

H-bridge circuit analysis: <https://goo.gl/gGTKzb>