

METE 3100U
Actuators and Power Electronics

Lecture 8
3-Phase Inverters


Outline of Lecture 8

By the end of today's lecture, you should be able to

- Understand the working principle of 3-phase inverters
- Control the voltage of a 3-phase inverter using PWM
- Develop a PWM controller for a 3-phase inverter

Applications

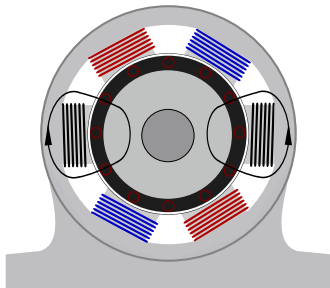Brushless motors used in drones are typically powered by PWM inverters. The windings are commutated to produce a rotating magnetic field that drags the rotor around.



How can a 3-phase signal be generated from a DC supply?

Applications


Three-phase electric power is a common method of alternating current electric power generation, transmission, and distribution.



DC current generated by solar farms needs to be converted into 3-phase AC for transmission.


3-phase inverters

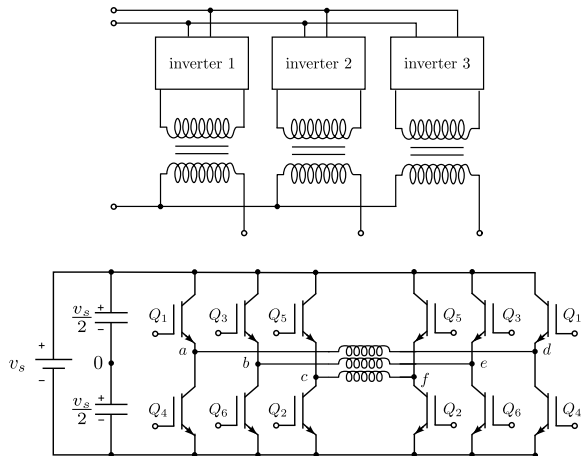Three single phase inverters are connected to form a 3-phase inverter



Half-bridge 3-phase inverter

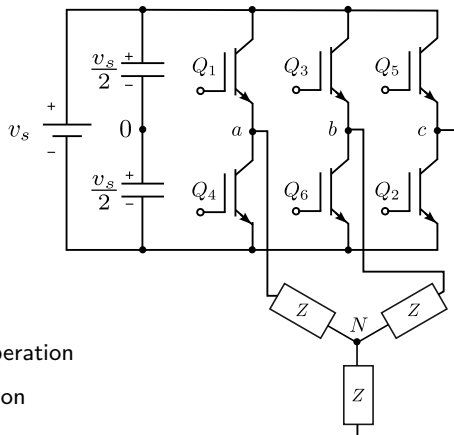The 3 arms are delayed by 120° to generate a three-phase AC supply.





Two modes of operation

→ 180° conduction

→ 120° conduction

180° phase conduction

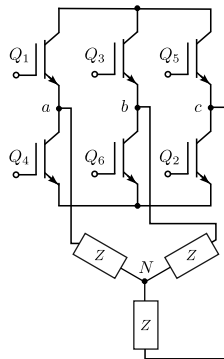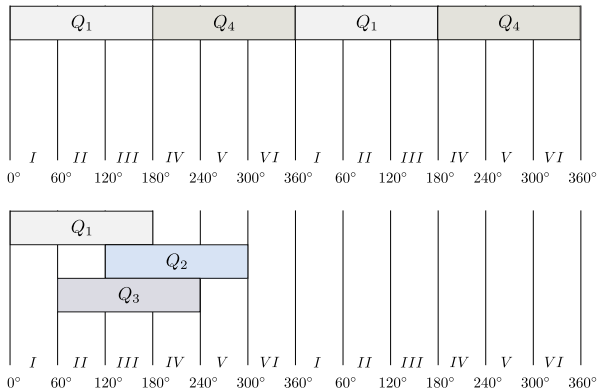

180° phase conduction

Transistors conducting in Phase I

→ Q_1 , Q_5 , and Q_6

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$

The voltage across the load is

$$v_{aN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$


$$v_{bN} = i_1 Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] Z = -\frac{2v_s}{3}$$
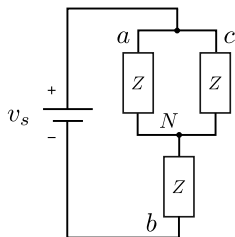
$$v_{cN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$



180° phase conduction

	Q ₁			Q ₄			Q ₁			Q ₄		
	Q ₆	Q ₃			Q ₆			Q ₃		Q ₆		
	Q ₅	Q ₂		Q ₅			Q ₂			Q ₅		
156	126	123	234	345	456	156						
I	II	III	IV	V	VI	I	II	III	IV	V	VI	
0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°

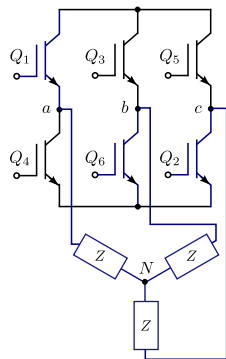


Transistors conducting in Phase II

→ Q₁, Q₂, and Q₆

The current is
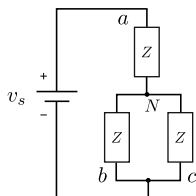
$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$



180° phase conduction

Transistors conducting in Phase II

→ Q_1 , Q_2 , and Q_6

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$

The voltage across the load is

$$v_{aN} = i_1 Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] Z = \frac{2v_s}{3}$$


$$v_{bN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$
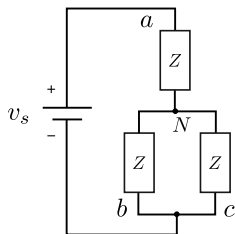
$$v_{cN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$



180° phase conduction

Q ₁			Q ₄			Q ₁		Q ₄				
Q ₆			Q ₃		Q ₆			Q ₃		Q ₆		
Q ₅		Q ₂		Q ₅			Q ₂		Q ₅			
156	126	123	234	345	456	156						
I	II	III	IV	V	VI	I	II	III	IV	V	VI	
0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°

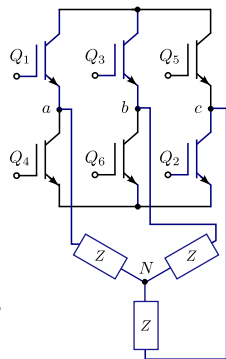


Transistors conducting in Phase III

→ Q₁, Q₂, and Q₃

The current is
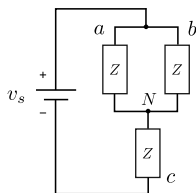
$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$



180° phase conduction

Transistors conducting in Phase III

→ Q_1 , Q_2 , and Q_3

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2 v_s}{3 Z}$$

The voltage across the load is

$$v_{aN} = \frac{i_1}{2} Z = \left[\frac{2 v_s}{3 Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$


$$v_{bN} = \frac{i_1}{2} Z = \left[\frac{2 v_s}{3 Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$
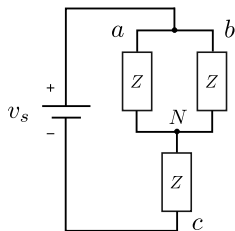
$$v_{cN} = i_1 Z = \left[\frac{2 (-v_s)}{3 Z} \right] Z = -\frac{2v_s}{3}$$



180° phase conduction

Q ₁				Q ₄			Q ₁			Q ₄		
Q ₆			Q ₃		Q ₆			Q ₃			Q ₆	
Q ₅	Q ₂			Q ₅			Q ₂			Q ₅		
156	126	123	234	345	456	156						
I	II	III	IV	V	VI	I	II	III	IV	V	VI	
0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°

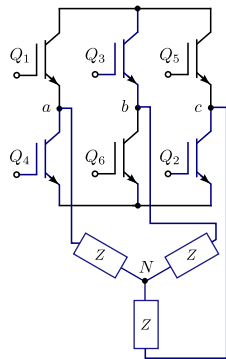


Transistors conducting in Phase IV

→ Q₂, Q₃, and Q₄

The current is
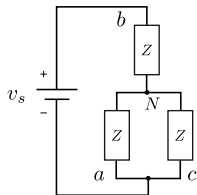
$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$



180° phase conduction

Transistors conducting in Phase IV

→ Q_2 , Q_3 , and Q_4

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$

The voltage across the load is

$$v_{aN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$


$$v_{bN} = i_1 Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] Z = \frac{2v_s}{3}$$
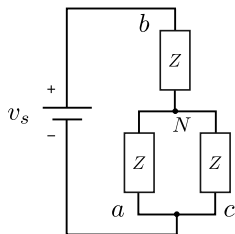
$$v_{cN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$



180° phase conduction

Q ₁			Q ₄			Q ₁			Q ₄			
Q ₆		Q ₃		Q ₆		Q ₃		Q ₆		Q ₃		
Q ₅	Q ₂			Q ₅	Q ₂			Q ₅	Q ₂			
156	126	123	234	345	456	156						
I	II	III	IV	V	VI	I	II	III	IV	V	VI	
0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°

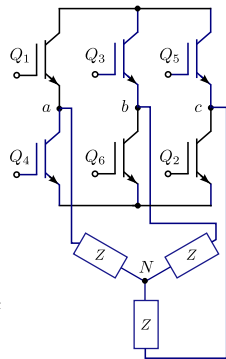


Transistors conducting in Phase V

→ Q₃, Q₄, and Q₅

The current is
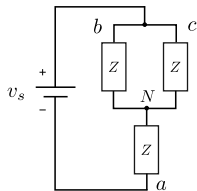
$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$



180° phase conduction

Transistors conducting in Phase V

→ Q_3 , Q_4 , and Q_5

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$

The voltage across the load is

$$v_{aN} = i_1 Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] Z = -\frac{2v_s}{3}$$


$$v_{bN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$
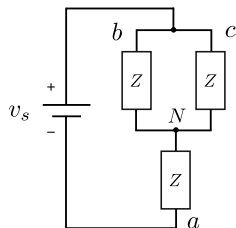
$$v_{cN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] \frac{Z}{2} = \frac{v_s}{3}$$



180° phase conduction

Q ₁			Q ₄			Q ₁			Q ₄			
Q ₆		Q ₃				Q ₆		Q ₃		Q ₆		
Q ₅	Q ₂			Q ₅	Q ₂			Q ₅				
156	126	123	234	345	456	156						
I	II	III	IV	V	VI	I	II	III	IV	V	VI	
0°	60°	120°	180°	240°	300°	360°	60°	120°	180°	240°	300°	360°

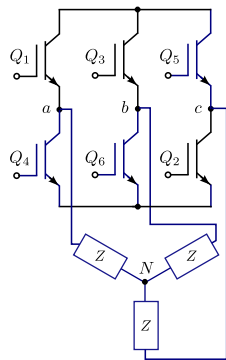


Transistors conducting in Phase VI

→ Q₄, Q₅, and Q₆

The current is
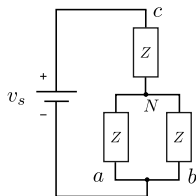
$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$



180° phase conduction

Transistors conducting in Phase VI

→ Q_4 , Q_5 , and Q_6

The current is


$$i_1 = \frac{v_s}{Z + \frac{Z}{2}} = \frac{2}{3} \frac{v_s}{Z}$$

The voltage across the load is


$$v_{aN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$

$$v_{bN} = \frac{i_1}{2} Z = \left[\frac{2}{3} \frac{(-v_s)}{Z} \right] \frac{Z}{2} = -\frac{v_s}{3}$$
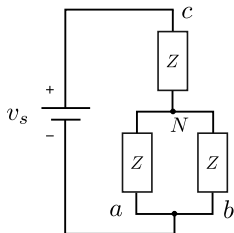
$$v_{cN} = i_1 Z = \left[\frac{2}{3} \frac{v_s}{Z} \right] Z = \frac{2v_s}{3}$$




Line to neutral waveforms

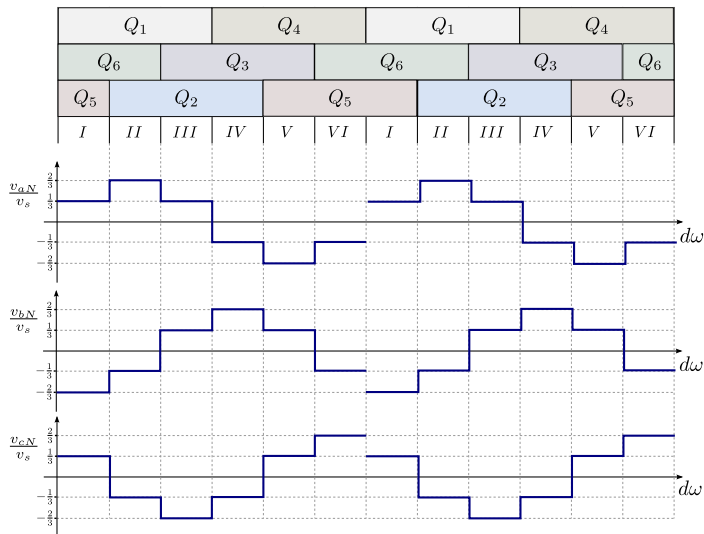


Line to line waveforms

$$V_{ab} = V_{aN} - V_{bN}$$

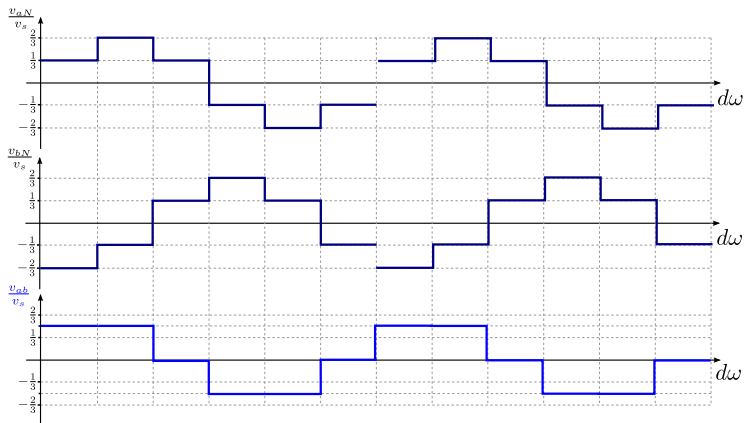


Line to line waveforms

$$V_{bc} = V_{bN} - V_{cN}$$

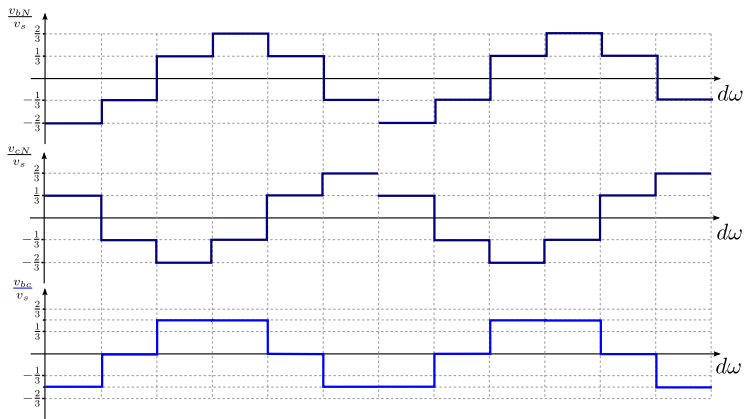

Line to line waveforms


$$V_{ac} = V_{aN} - V_{cN}$$

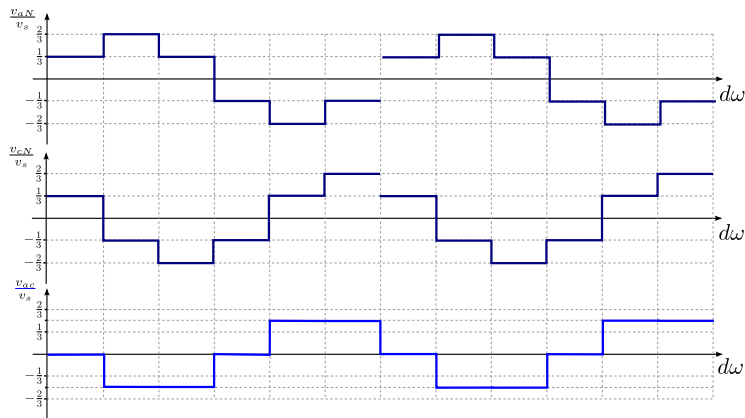

Line to neutral and line to line voltages are shifted by 60° .

Space vector modulation

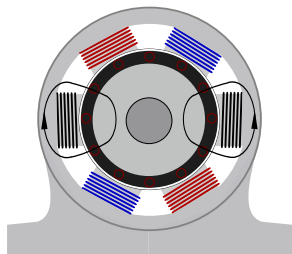In brushless motor, the windings are commutated to produce a rotating magnetic field that drags the rotor around.



Can it be powered by a 3-phase inverter?


→ There are only six different voltage angles available.

→ To rotate a motor, a smoothly rotating voltage vector is required.

Space vector modulation


→ Transistor in the same leg cannot be activated at the same time

→ There are 8 possible combinations

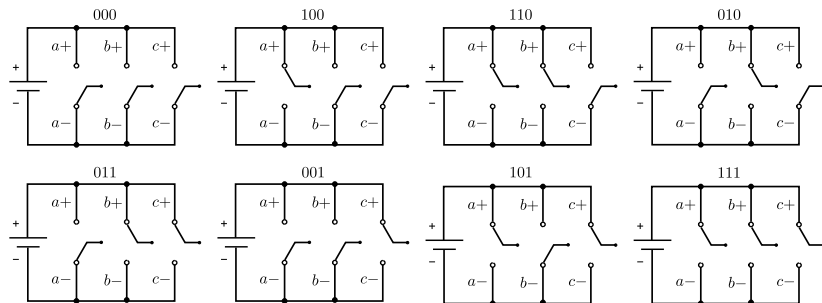

Space vector modulation

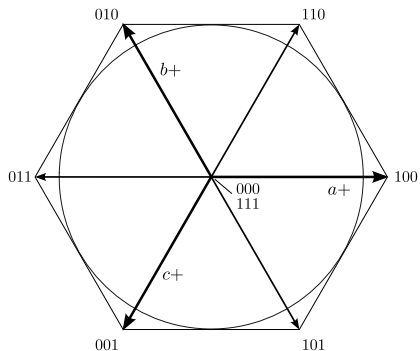
Possible switching vectors for a 3-phase inverter using space vector modulation



000	100	110	010	011	001	101	111
zero	+a	-c	+b	-a	+c	-b	zero

Synthesizing output voltage


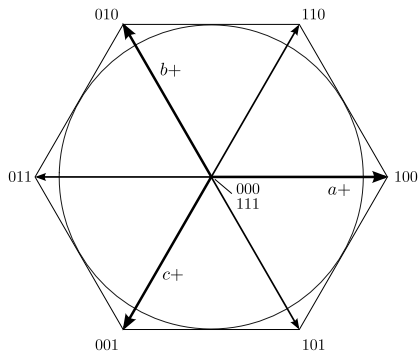
Possible switching vectors for a 3-phase inverter using space vector modulation



000	100	110	010	011	001	101	111
zero	+a	-c	+b	-a	+c	-b	zero

Synthesizing output voltage

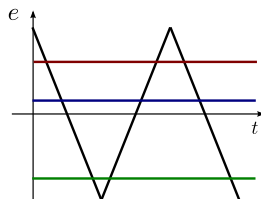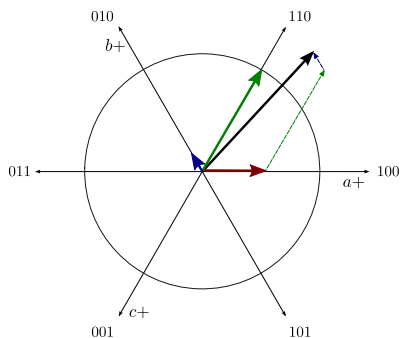Objective: Follow a reference vector signal using 3 different voltages and angles




000	100	110	010	011	001	101	111
zero	+a	-c	+b	-a	+c	-b	zero

Vectors will have to be switched between $a+$, $c-$, and $b+$

Synthesizing output voltage

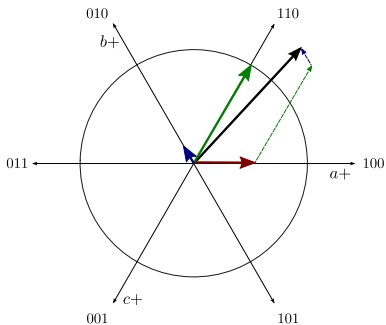
PWM is used to create the desired voltage vector



The sequence of activation is


000 100 110 111 110 100 000

<https://youtu.be/X1cqUuKqOH8>

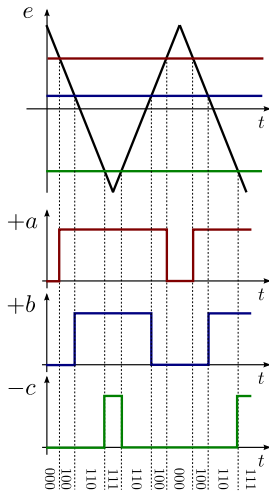

Synthesizing output voltage


Example 2

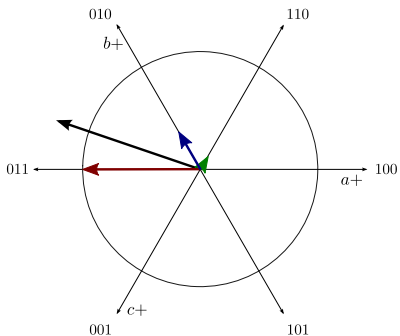

The sequence of activation is


000 010 011 111 011 010 000

Note: the pulse width varies

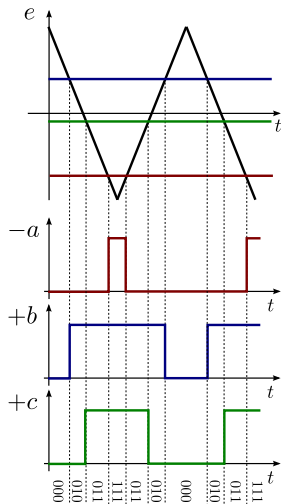


Exercise 33

The sinusoidal **phase-to-neutral** voltage of the 3-phase inverter are shifted by 120° . Calculate the line currents in the load due to the fundamental component of the output voltage.

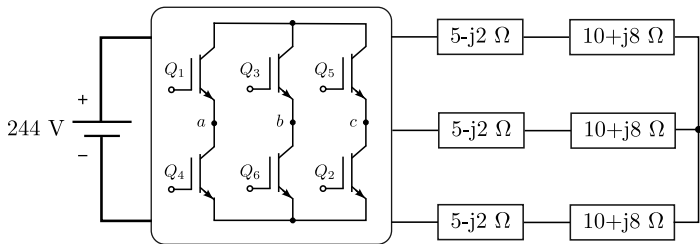


Exercise 33 - continued

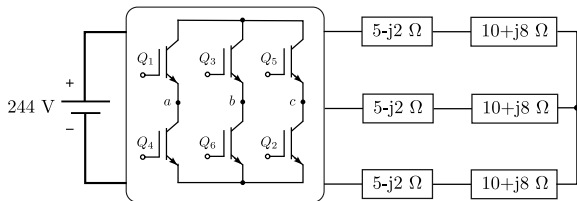

Exercise 33 - continued

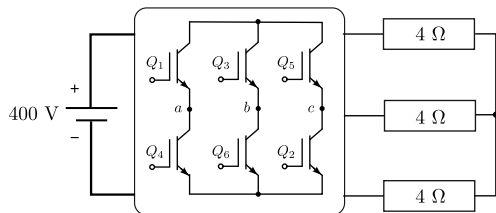Exercise 34


The DC input voltage of the 3-phase inverter is 400 V and the load is $Z = 4 \Omega$.



Calculate:

- The instantaneous voltage levels of the line to-neutral-voltage
- The peak current in each transistor



Exercise 34 - continued

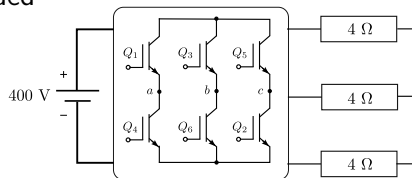



Exercise 34 - continued

Exercise 35

Determine the transition sequence of the state vector that are required to modulate the reference voltage vector shown.

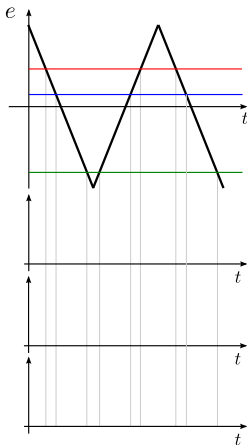
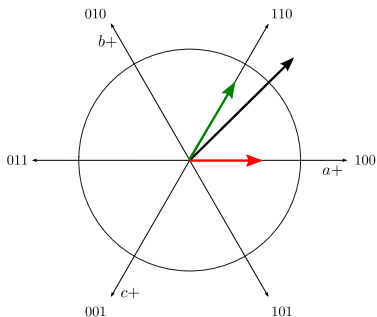


Exercise 35 - continued

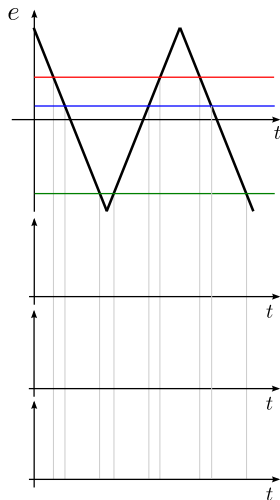
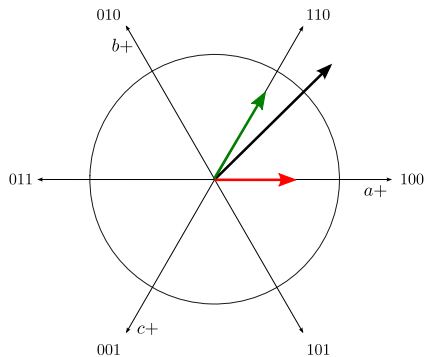


Exercise 36

Determine the transition sequence of the state vector that are required to modulate the reference voltage vector shown.

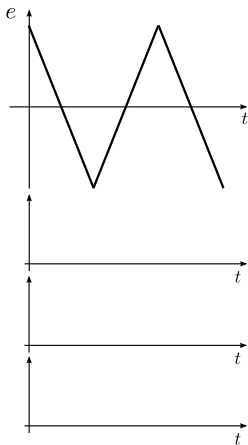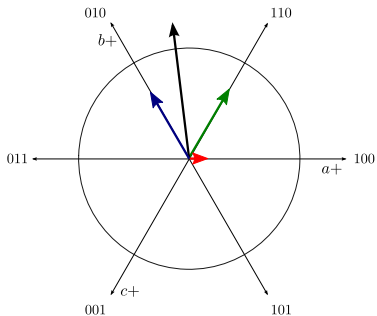

Exercise 36 - continued

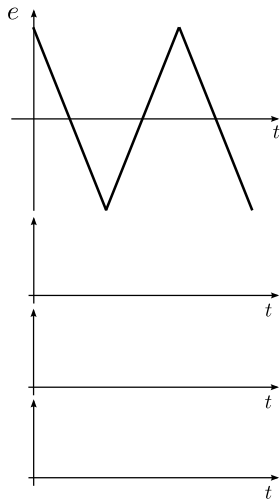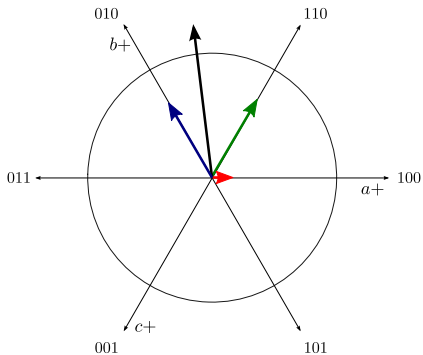

Exercise 37

- (a) What is an inverter ?
- (b) What is the principle of operation of an inverter?
- (c) What are the performance parameters of inverter?
- (d) What is space vector modulation?
- (e) What is a boost-inverter (step up)?
- (f) What is the voltage gain of a boost inverter ?
- (g) What are the reason for adding a filter on an inverter output?
- (h) What is the phase shift in a 180° conduction 3-phase inverter?
- (i) What is sinusoidal PWM?
- (j) What is the difference between unipolar and bipolar PWM?

Next class...

- Electromagnetic energy conversion

Additional supporting materials for Lecture 8:

Space vector modulation: <https://bit.ly/2C5QAfu>

120° conduction: <https://youtu.be/w6BIs3MZhUM>